


# Numerical Analysis

## Homework 3. Resistor Networks


**Due: March 21, 2017**

Please formulate and solve the following resistor network problems.

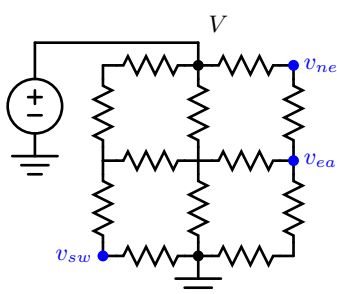
1. Assuming each resistor is  $1\text{ K}\Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



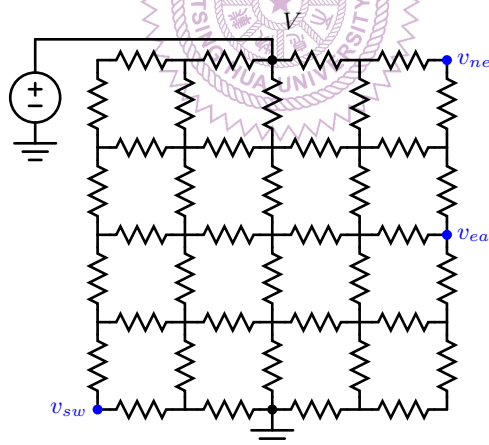
2. Assuming each resistor is  $500\text{ }\Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



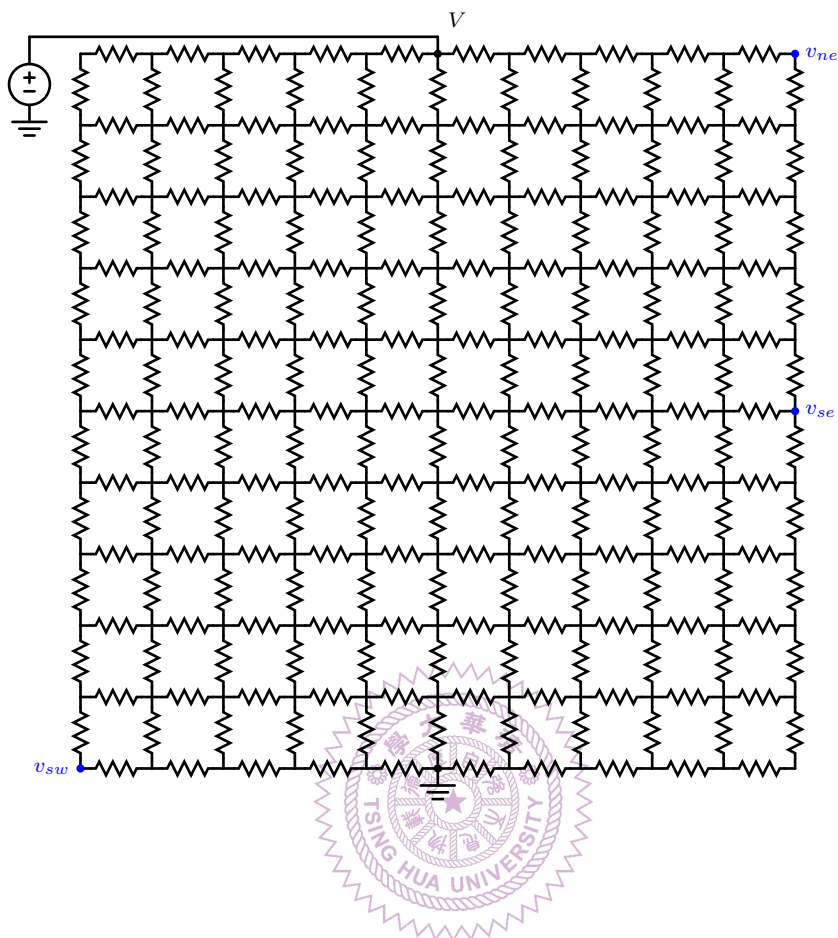3. Assuming each resistor is  $200\ \Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



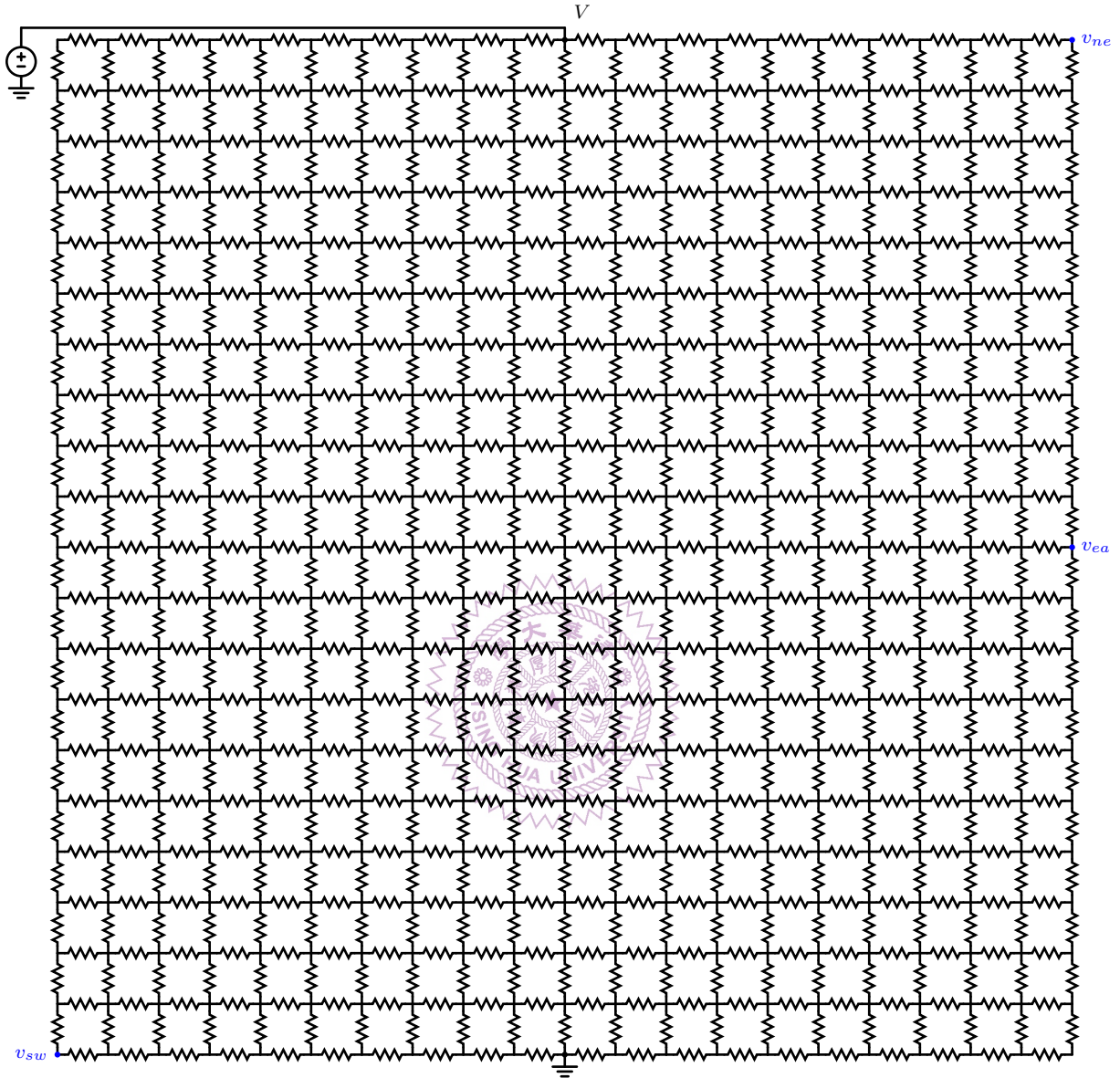4. Assuming each resistor is  $100\ \Omega$  and the voltage,  $V$ , is 1 volt, please find the equivalent resistance of the network and the three voltage values,  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$ .



5. Assuming that the resistor mesh has 40 resistors per side and each resistor is  $50\ \Omega$ . The 1-Volt voltage source is connected to the center of the north side and the center of south side is grounded.  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$  is the voltage value for the north-east corner, center of east side and south-west corner, respectively. Please find the equivalent resistance and the voltages of those three nodes.
6. Assuming that the resistor mesh has 50 resistors per side and each resistor is  $40\ \Omega$ . The 1-Volt voltage source is connected to the center of the north side and the center of south side is grounded.  $v_{ne}$ ,  $v_{ea}$  and  $v_{sw}$  is the voltage value for the north-east corner, center of east side and south-west corner, respectively. Please find the equivalent resistance and the voltages of those three nodes.

7. Please state your observations after solving all six questions.

### Notes.

1. For this homework you need to turn in a **C++** program that solves the resistor network problem for question 6. If your program is parametrized then it can solve for all 6 problems using command line arguments. For example,

```
$ ./a.out 10
```

to solve question 3 that each linear dimension has 10 resistors. If your program is not parametrized, then turn in the one that solves question 6. Name your program `hw03.cpp`.

2. A `pdf` file is also needed. Please name this file `hw03a.pdf`.
3. Submit your files on EE workstations. Please use the following command to submit your homework 3.

```
$ ~ee407002/bin/submit hw03 hw03a.pdf hw03.cpp MAT.h MAT.cpp VEC.h VEC.cpp
```

where `hw03` indicates homework 3.

4. Your report should be clearly written such that I can understand it. The writing, including English grammar, is part of the grading criteria.