

Numerical Analysis

Homework 12. RLC Circuit.

102061125 Kuan-Chun Chen

1. Objective

The RLC circuit is shown below.

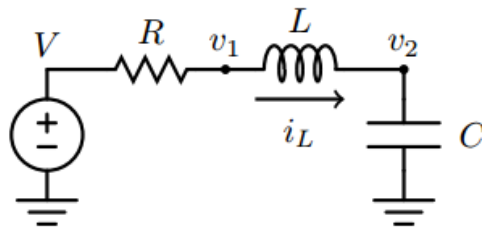


Figure 1. RLC circuit

Using these equations to solve v_1 , v_2 and i_L :

$$\frac{v_1 - V}{R} + i_L = 0,$$

$$\frac{dv_2}{dt} = \frac{i_L}{C},$$

$$\frac{di_L}{dt} = \frac{v_1 - v_2}{L}.$$

And assuming

- (1) $V(t) = 1$ for all t ,
- (2) at $t = 0$, $v_1(0) = 1$, $v_2(0) = 0$, and $i_L(0) = 0$,
- (3) $R = 1 \, \Omega$, $L = 1$ Henry, and $C = 1$ Farad.

2. Approach

Algorithm. Methods for solving ODEs with a given initial value.

Forward Euler Method

$$x(t + h) = x(t) + h \cdot f(t)$$

Backward Euler Method

$$x(t + h) = x(t) + h \cdot f(t + h, x(t + h))$$



Trapezoidal Method

$$x(t + h) = x(t) + h \cdot \frac{f(t + h, x(t + h)) + f(t, x(t))}{2}$$



3. Results

3.1. Plot

Forward Euler

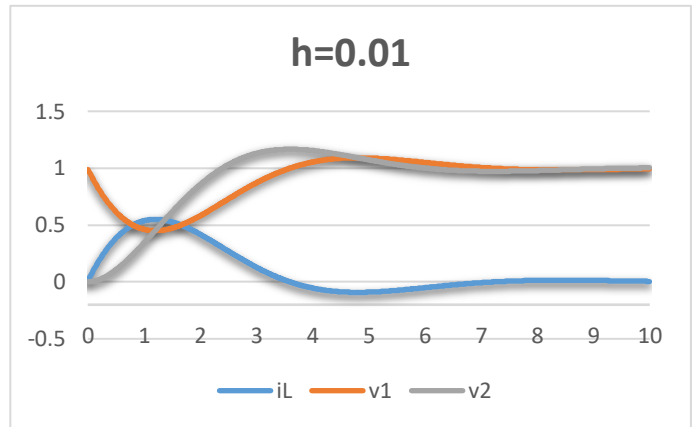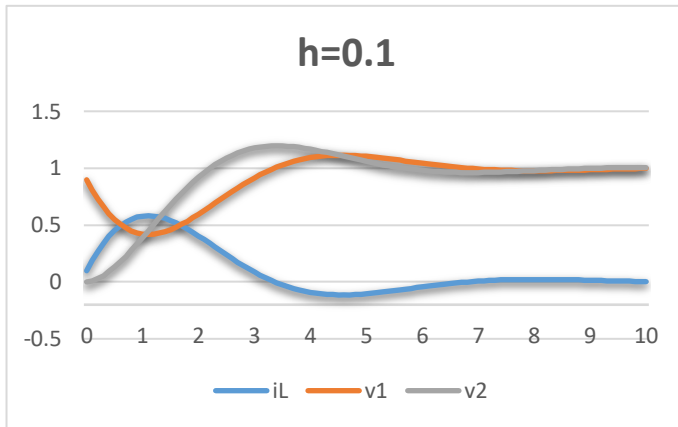

Backward Euler

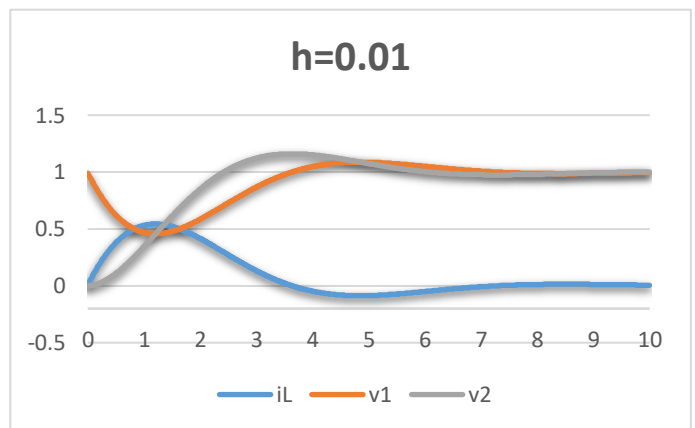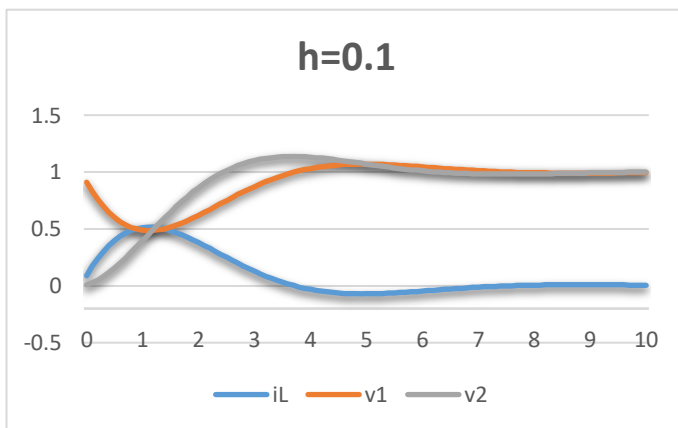

Trapezoidal

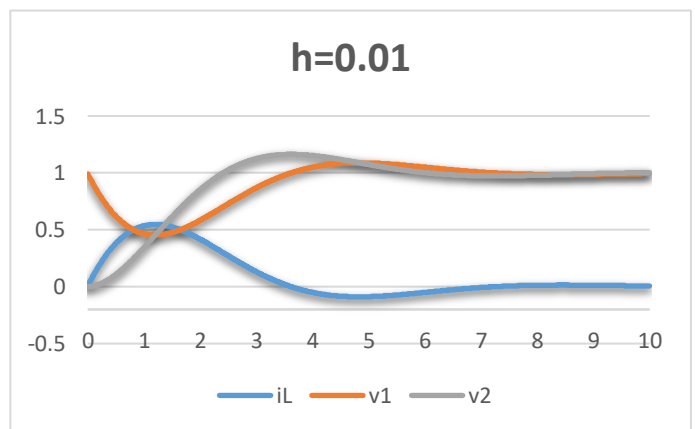
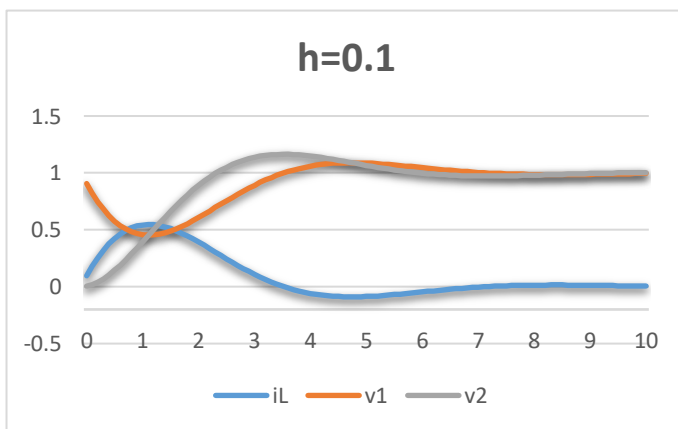


Table 1.

3.2. Maximum and minimum

h=0.1				h=0.01		
Forward Euler						
	v₁	v₂	i_L	v₁	v₂	i_L
max	1.1139	1.19627	0.581654	1.09125	1.16602	0.549617
min	0.418346	0	-0.11391	0.450383	0	-0.09125
Backward Euler						
	v₁	v₂	i_L	v₁	v₂	i_L
max	1.07026	1.13651	0.515275	1.08694	1.16011	0.543012
min	0.484725	0.009009	-0.07026	0.456988	9.9e-05	-0.08694
Trapezoidal						
	v₁	v₂	i_L	v₁	v₂	i_L
max	1.08936	1.16346	0.546816	1.08907	1.16304	0.546298
min	0.453184	0.004751	-0.08936	0.453702	4.98e-05	-0.08907

Table 2.

4. Observations

4.1. Different in method (same in h, variable)

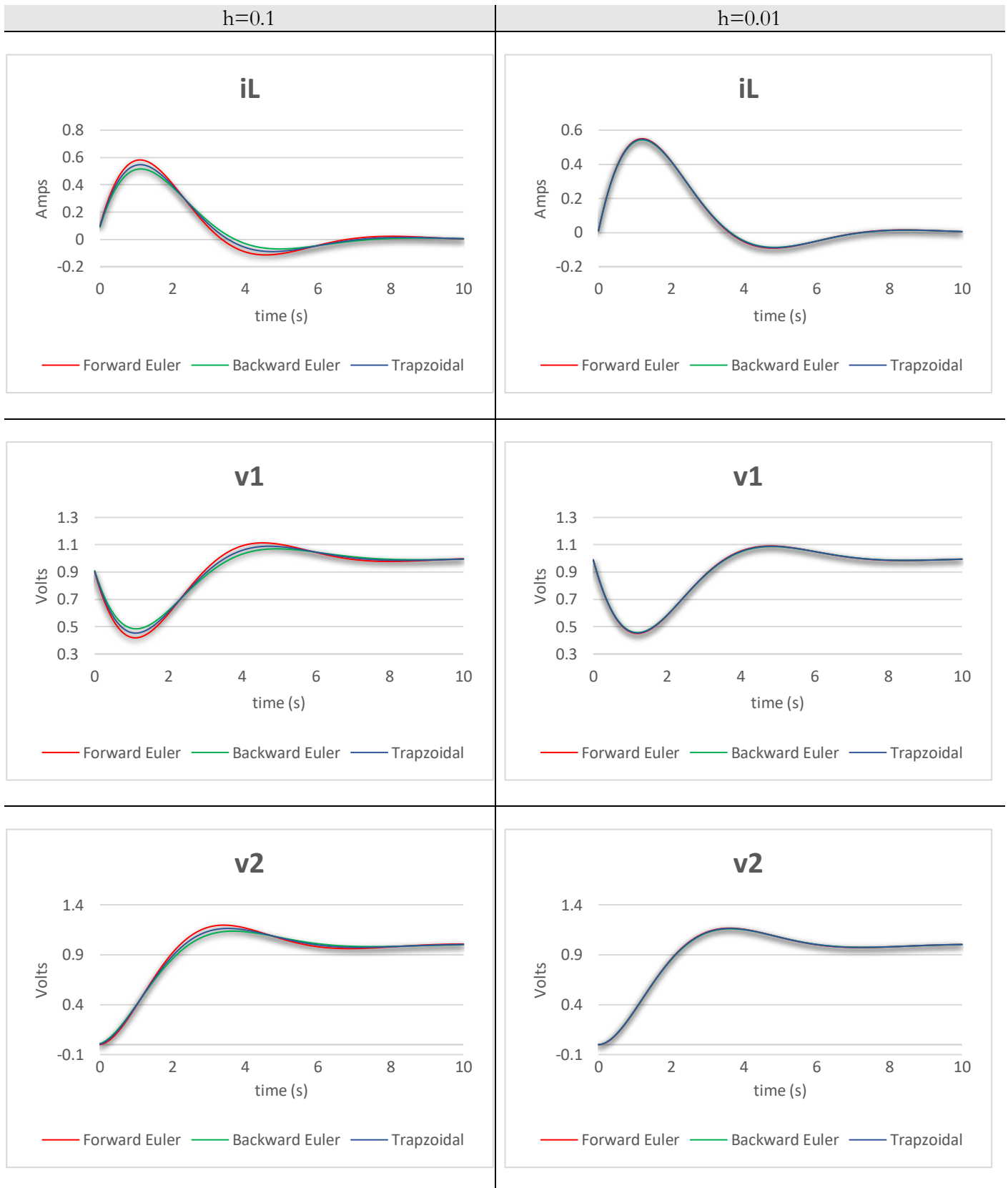


Table 3.

4.2. Different in h (same in method, variable)

- Forward Euler

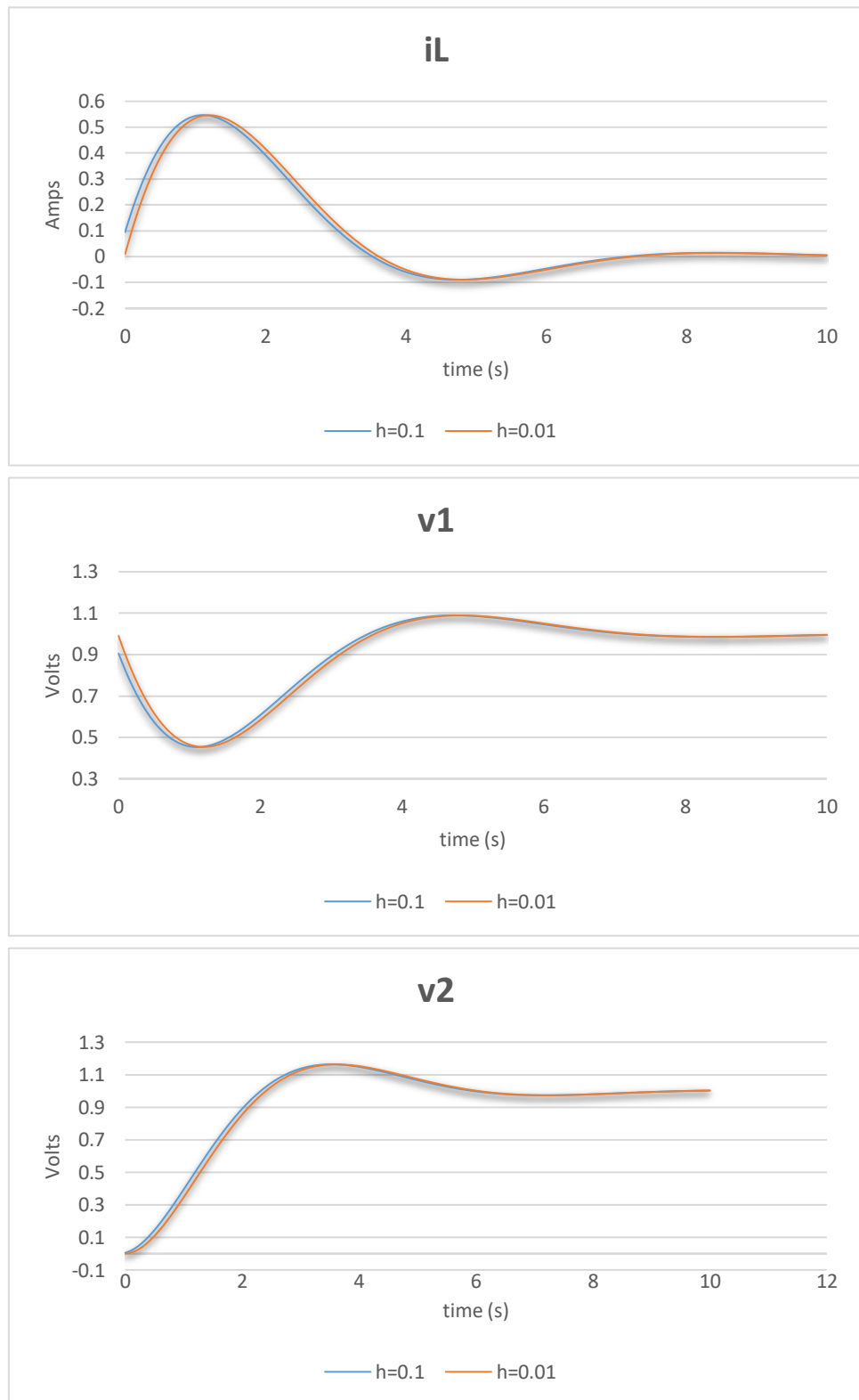


Table 4.

- **Backward Euler**

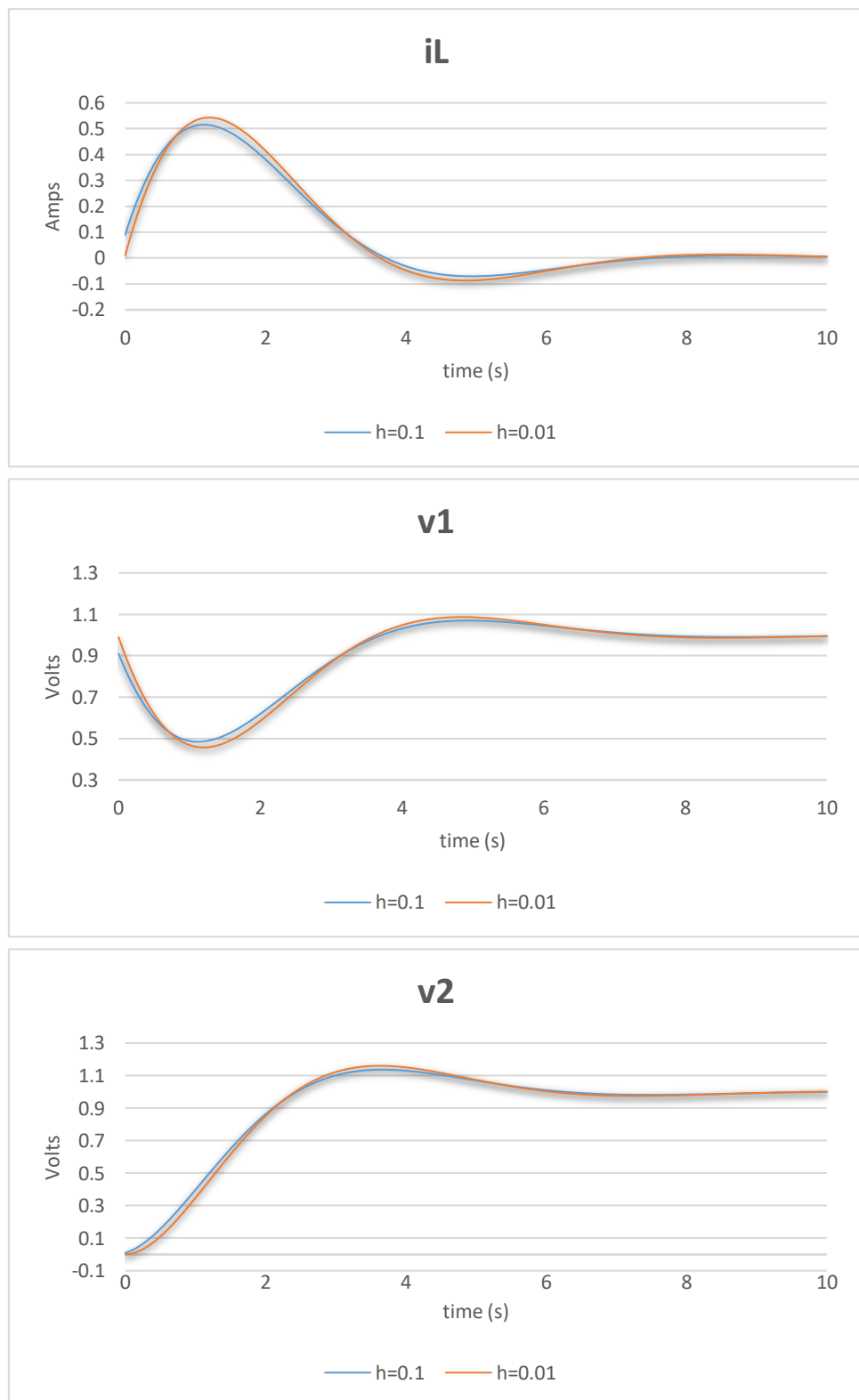


Table 5.

- Trapezoidal

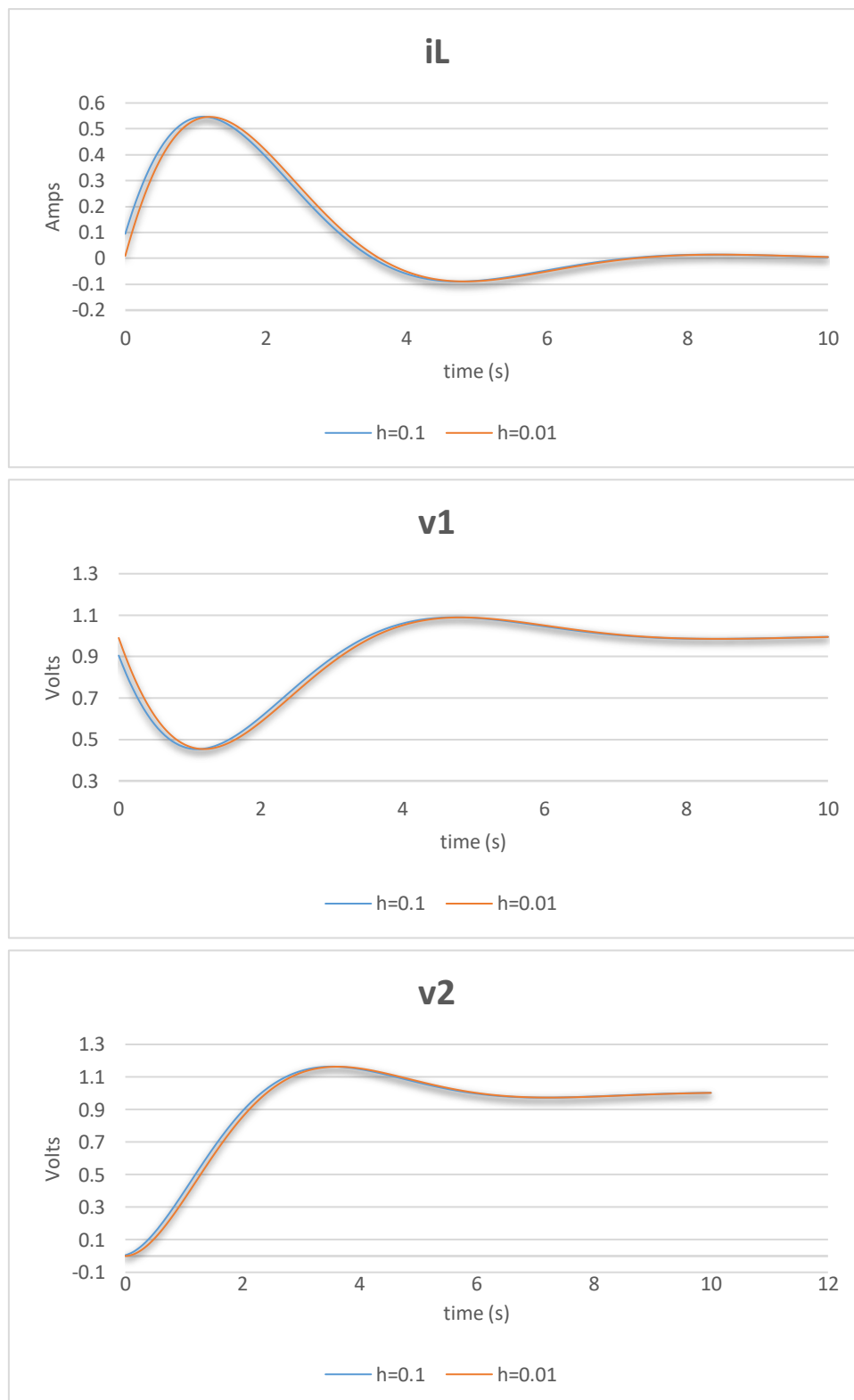


Table 6.

4.3. Conclusion

- Amplitude

For $h=0.1$ and 0.01 , from Table 2 and Table 3 we can obviously see the amplitude in damped oscillation region:

$$\text{Forward Euler} > \text{Trapezoidal} > \text{Backward Euler}$$

- Forward Euler

From Table 2 and Table 4, the amplitude in damped oscillation region is **smaller** when h is smaller.

- Backward Euler

From Table 2 and Table 5, the amplitude in damped oscillation region is **larger** when h is smaller.

- Trapezoidal

From Table 2 and Table 6, the amplitude in damped oscillation region is **smaller** when h is smaller.